

## Content

Introduction .....	1
MC34063.....	2
Description .....	2
Block Diagram Description .....	3
Pin Configuration .....	4
Step-down Converter.....	4
Results .....	5
Description .....	5
Step-down converter circuit .....	5
Step-down Diagram.....	6
Result .....	6
Discussion .....	6
Step-up converter .....	10
Result .....	10
Discussion .....	10
Step-up converter circuit .....	10
Step-up Diagram .....	11
Results .....	11
Discussion .....	11
Buck Converter Design .....	14
Results .....	18
Discussion .....	19
Buck Converter Circuit .....	22
Conclusions .....	24
Reflections.....	24
Referencing .....	24

## Introduction

In this report, we will study MC34063 IC and we will use MC34063 design a Buck converter.

MC34063 is a 1.5A Step up or step down or inverting regulator, due to DC voltage conversion property, MC34063 is a DC-DC converter IC.

☑ This IC provides following features in its 8pin package

☑ Temperature compensated reference

☑ Current limit circuit

☑ Controlled Duty cycle oscillator with an active high current driver output switch.

☑ Accept 3.0V to 40V DC.

☑ Can be operated at 100 kHz switching frequency with a 2% tolerance.

☑ Very low Standby current

☑ Adjustable output voltage

☑ Also, despite these features, it is widely available and it is much cost efficient than other ICs available in such segment.

This report includes 4 parts: first, we will conclude MC34063 features and functions. Second, we will simulate and test step up converter circuit given in the datasheet. Third, we will simulate and test step down converter circuit given in the datasheet. Fourth, we will design a buck converter circuit.

## MC34063


### Description

The MC34063A/E series is a monolithic control circuit delivering the main functions for DC-DC voltage converting. The device contains an internal temperature compensated reference, comparator, duty cycle is controlled oscillator with an active current limit circuit, driver and high current output switch. Output voltage is adjustable through two external resistors with a 2% reference accuracy. Employing a minimum number of external components the MC34063A/E devices series is designed for Step-Down, Step-Up and Voltage-Inverting applications.

### Features

- ☑ This IC provides following features in its 8pin package-
- ☑ Temperature compensated reference
- ☑ Current limit circuit
- ☑ Controlled Duty cycle oscillator with an active high current driver output switch.
- ☑ Accept 3.0V to 40V DC.
- ☑ Can be operated at 100 kHz switching frequency with a 2% tolerance.
- ☑ Very low Standby current
- ☑ Adjustable output voltage
- ☑ Also, despite these features, it is widely available and it is much cost efficient than other ICs available in such segment.

Below image is the internal circuit of MC34063 is shown- Black Diagram.

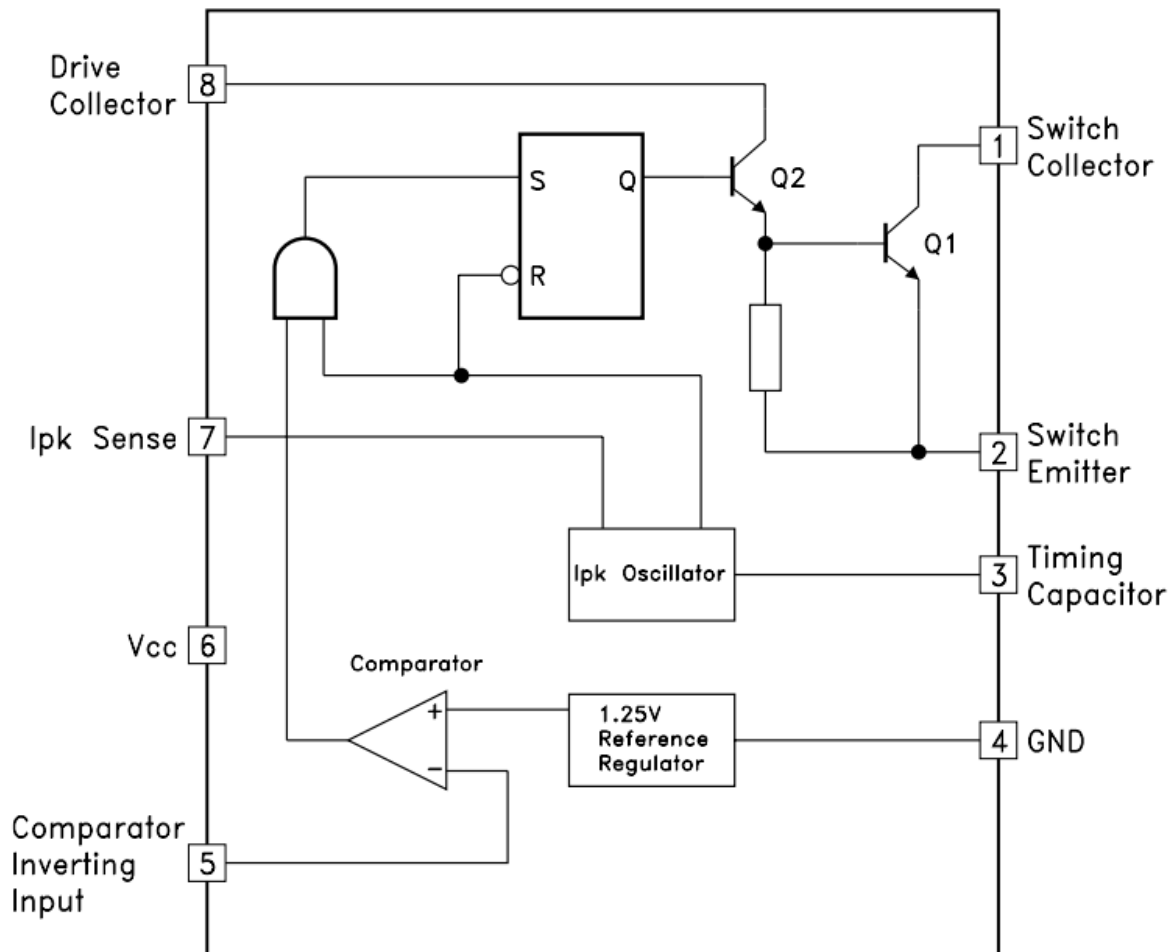

*Figure 1 Black Diagram*

### Black Diagram Description

Inverting Input of Comparator (Pin 5 CII) monitors the output voltage ( $V_{out}$ ) through two external voltage divide resistors. From Figure 1, we know the reference voltage is 1.25V, it is constant. Pin 3 Timing capacitor recharged and discharged in order to produce oscillation. Recharging and discharging current is constant, oscillation frequency and switch on-off time depend on Pin 3 external timing capacitor. When Pin 5 input voltage larger than 1.25, Pin1 and Pin 2 turn on. Source recharge output capacitor and inductor. In contrast, Pin 2 and Pin1 turn off, the inductance recharged capacitor.

Between Pin 6 and Pin7 external resistor, through testing resistor voltage drop realizes current limit. When testing resistor voltage drop nears 0.3V, current limit circuit operates, through Pin 3 oscillation recharging timing capacitor quickly to reduce recharging time and Pin 2 switch turn on time, then extending Pin 2 switch turn off time. If Pin 8 and Pin 2 external ground. T2 will have higher voltage drop, to prevent higher voltage, Pin 8 and Pin 2 external resistor and inductor.

### Pin Configuration

The pin configuration of the MC34063 DC to DC converter is shown below. This IC includes 8-pins where each pin with its functionality is discussed below. MC34063 pin out diagram has been shown in the below image.

#### CONNECTION DIAGRAM (top view)

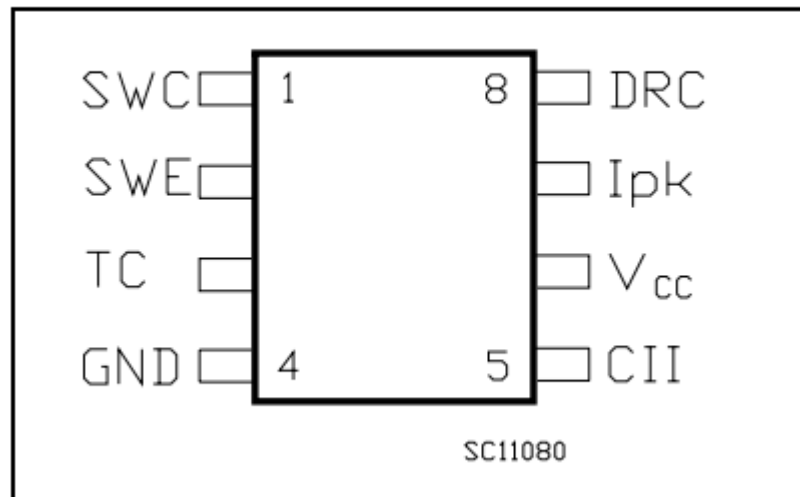


Figure 2 Pin Configuration Diagram

Pin No	Symbol	Name	Function
1	SWC	Switch Collector	Switch collector pin of the transistor which is also known as an o/p voltage pin.
2	SWE	Switch Emitter	Switch emitter pin of the transistor
3	TC	Timing Capacitor	This pin is connected to a capacitor to decide the switching frequency
4	GND	Ground	This pin is connected to the GND pin
5	CII	Inverting Input of Comparator	This pin is used to set the o/p voltage
6	$V_{cc}$	Input Voltage	Input voltage is given to this pin
7	$I_{pk}$	$I_{pk}$ Sense	This pin is used to set the o/p current
8	DRC	Driver Collector	This is the collector pin of the transistor

Chart 2 Pin Configuration Function

### Step-down Converter

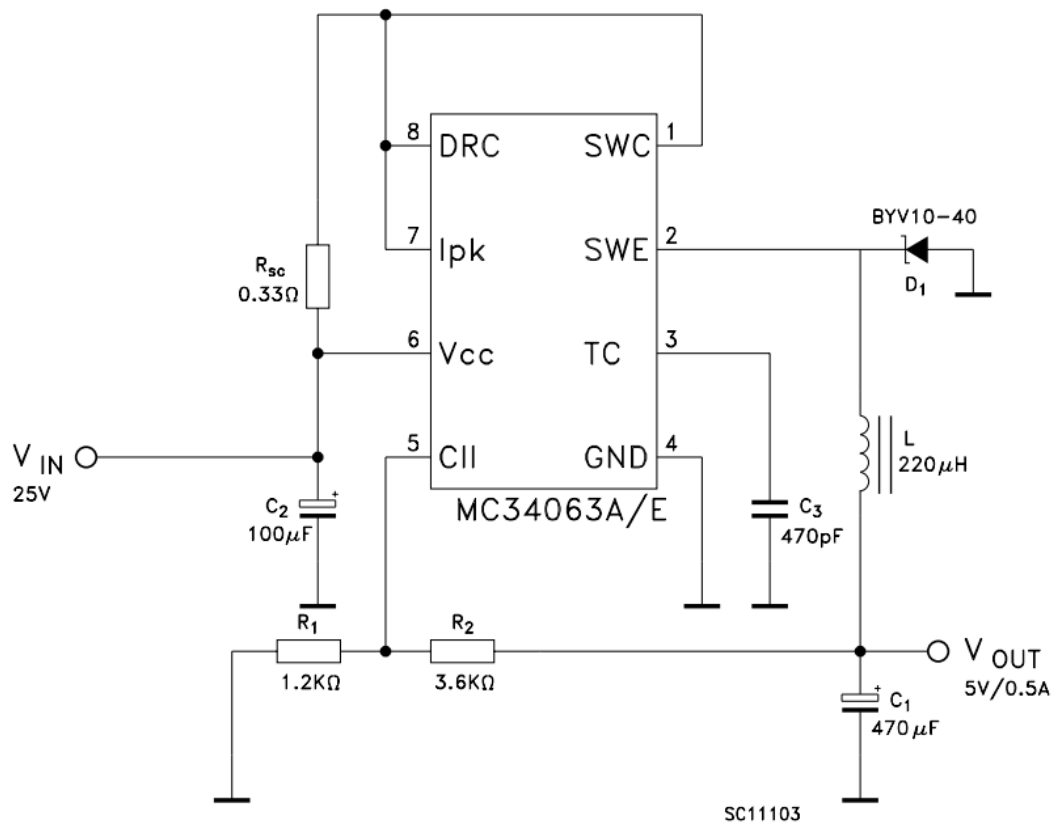


Figure 3 Step-down Converter Circuit of Datasheet

## Results

This is a MC 34063 step-down coverter circuit, input voltage ( $V_{in}$ ) is 25V, through the step-down circuit, the output voltage ( $V_{out}$ ) is 5V.

## Description

### Step-down converter circuit

Inverting Input of Comparator (Pin 5 CII) monitors the output voltage ( $V_{out}$ ) through two external voltage divide resistors  $R_1$  and  $R_2$ .  $V_{out} = 1.25 * (1 + \frac{R_2}{R_1})$ . From Figure 1, we know the reference voltage is 1.25V, it is constant. Pin 3 Timing capacitor recharged and discharged in order to produce oscillation. Recharging and discharging current is constant, oscillation frequency and switch on-off time depend on Pin 3 external timing capacitor. When Pin 5 input voltage larger than 1.25, Pin1 and Pin 2 turn on. Source recharge output capacitor and inductor. In contrast, Pin 2 and Pin1 turn off, the inductor recharged capacitor.

Between Pin 6 and Pin7 is  $R_{sc}$ , through testing  $R_{sc}$  voltage drop realizes current limit. When testing resistor voltage drop nears 0.3V, current limit circuit operates, through Pin 3 ocsillation recharging timing capacitor quickly to reduce recharging time and Pin 2 switch turn on time, then extending Pin 2 switch turn off time. Pin 8 and Pin 2 external resistor and inductor to prevent higher voltage drop.

## Step-down Diagram

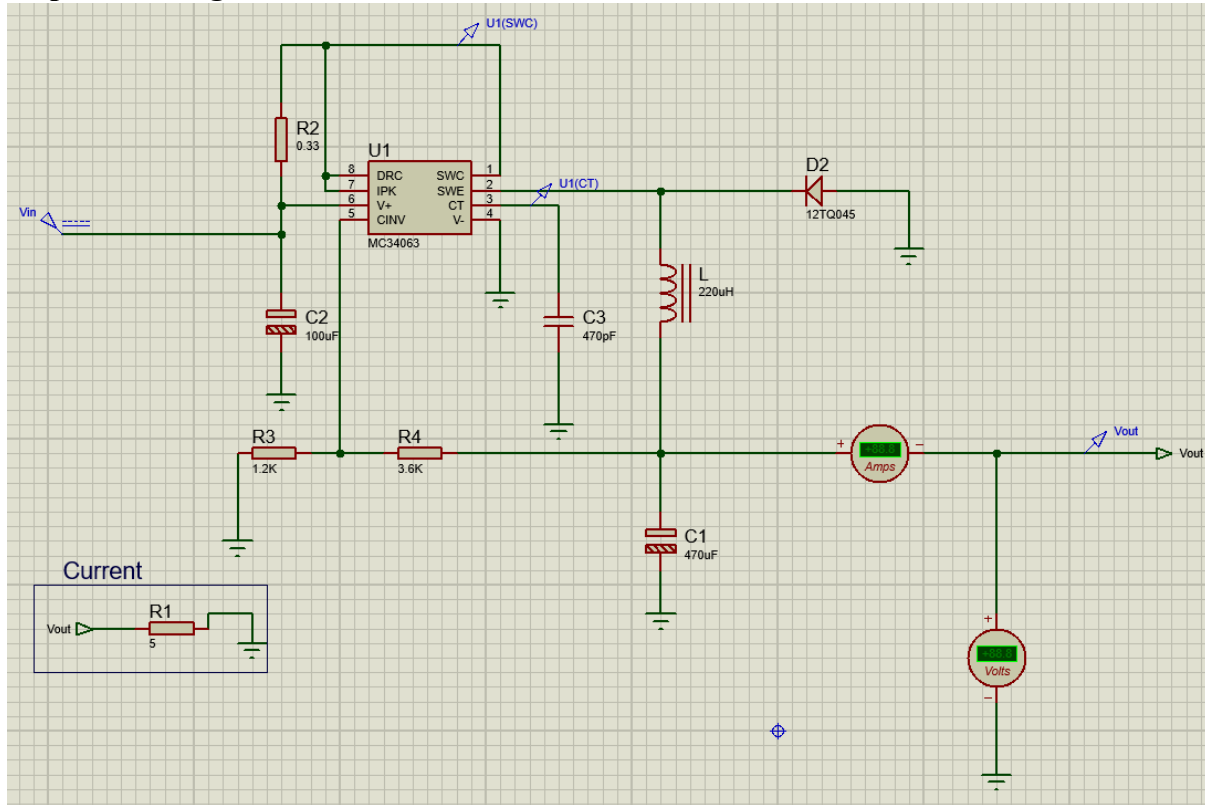


Figure 4 Step-down Proteus Diagram

## Result

This is a MC 34063 step-down coverter circuit Proteus Diagram, input voltage ( $V_{in}$ ) is 25V, through the step-down circuit, the output voltage ( $V_{out}$ ) is 5.05V.

## Discussion

Inverting Input of Comparator (Pin 5 CII) monitors the output voltage ( $V_{out}$ ) through two external voltage divide resistance ( $R_3$  and  $R_4$ )  $V_{out} = 1.25 * (1 + \frac{R_4}{R_3})$ , from Figure 1, we know the reference voltage is 1.25V, it is constant. Pin 3 Timing capacitor recharged and discharged in order to produce oscillation. Recharging and discharging current is constant, oscillation frequency depends on Pin 3 external timing capacitor. When Pin 5 input voltage larger than 1.25, Pin1 and Pin 2 turn on. Source recharge  $C_1$  and  $L$ ,. In contrast, Pin 2 and Pin1 turn off, the inductor ( $L$ ) recharged capacitor ( $C_1$ ).

Between Pin 6 and Pin7 is  $R_2$ , through testing  $R_2$  voltage drop realizes current limit. When testing  $R_2$  voltage drop nears 0.3V, current limit circuit operates, through Pin 3 oscillation recharging timing capacitor quickly to reduce recharging time and Pin 2 switch turn on time, then extending Pin 2 switch turn off time. Pin 8 and Pin 2 external resistor and inductor to prevent higher voltage.

From the Figure 5 and Figure 7, when time = 200.023ms,  $V_{CT} = 1.29V$ ,  $V_{out} = 5.04V$ ,  $V_{swc} = 25V$ , switch turn on, source ( $V_{in}$ ) recharge  $C_1$  and  $L$ ,  $V_{out}$  increased. When time = 200.052ms, the circuit produced voltage drop,  $V_{swc}$  reduced. When time = 200.062ms,  $V_{CT} = 1.36V$ ,  $V_{out} = 5.07V$ ,  $V_{swc} = 24.6V$ , since voltage drop =  $25 - 24.6 = 0.4V$  nears 0.3V, current limit circuit operates, through Pin 3 oscillation recharging timing capacitor quickly to reduce

recharging time and Pin 2 switch turn on time, then extending Pin 2 switch turn off time. Switch turn off suddenly,  $V_{out}$  suddenly drop (between time = 200.062ms and time = 00.068ms), the inductor (L) recharged capacitor ( $C_1$ ),  $V_{out}$  slowly drop. When time = 200.097ms,  $V_{CT} = 1.27V$ ,  $V_{out} = 5.04V$ ,  $V_{swc} = 25V$ , switch turn on, source ( $V_{in}$ ) recharge  $C_1$  and L,  $V_{out}$  increased.

$$T_{on} + T_{off} = 1 / (200.105 - 200.079) = 38\mu s \text{ (from Figure 6)}$$

$$V_{ripple} = \frac{I_{pk(switch)} * (T_{on} + T_{off})}{8 * C_o}$$

$$V_{ripple} = \frac{1 * 38 * 10^{-6}}{8 * 470 * 10^{-6}}$$

$$V_{ripple} = 0.01V$$

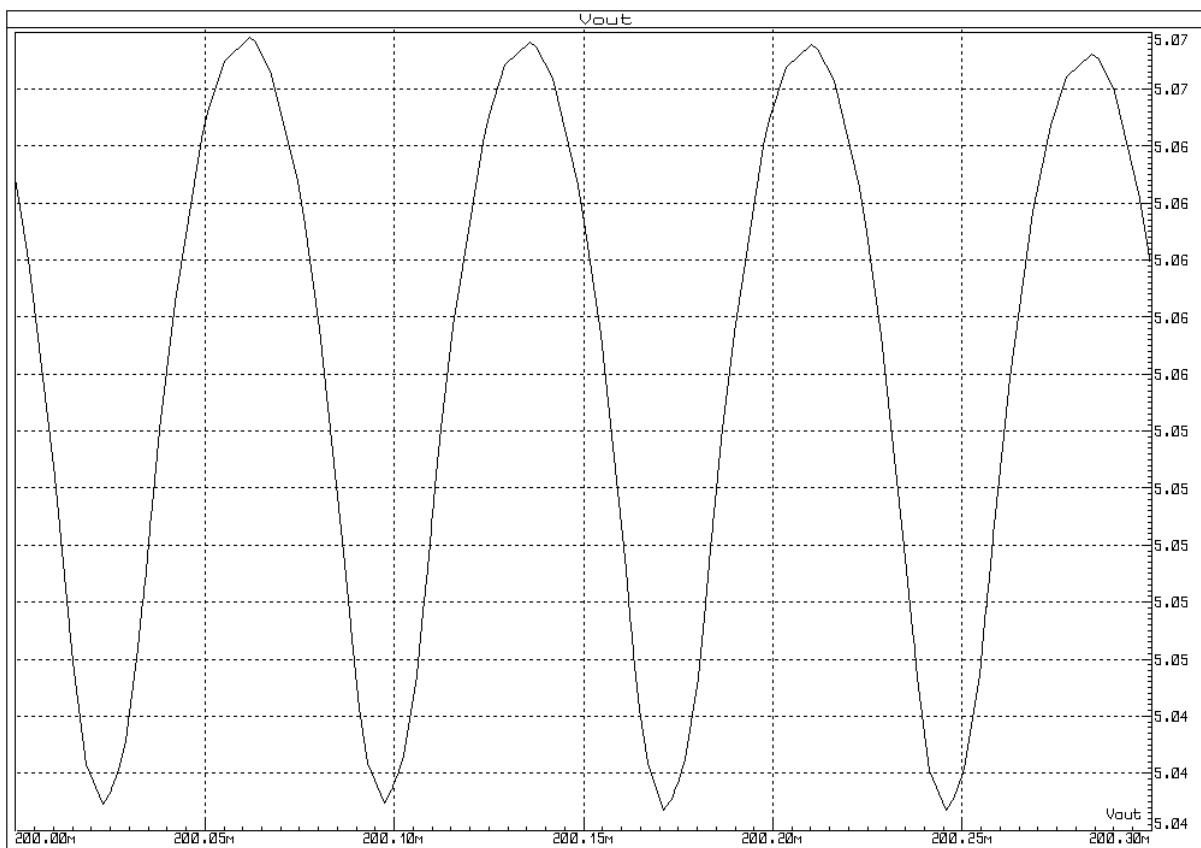


Figure 5  $V_{out}$  Analog Graph



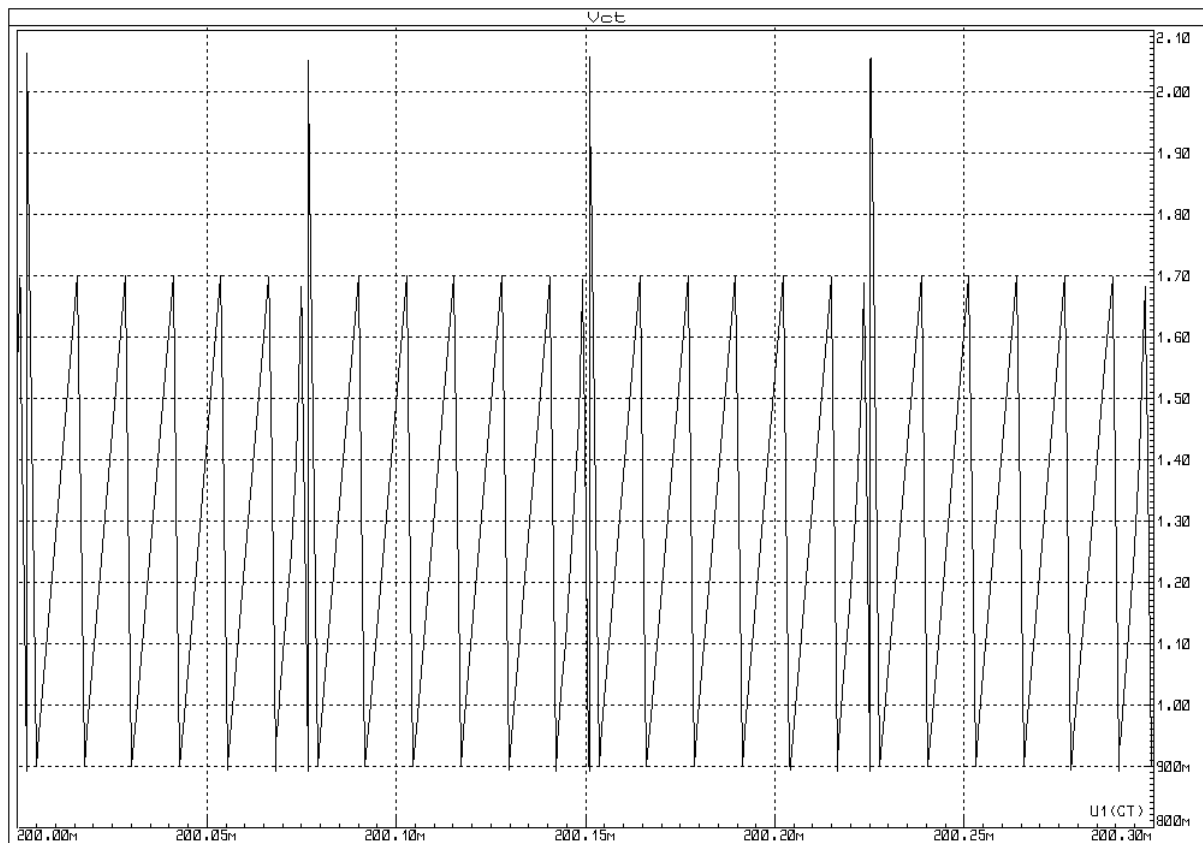


Figure 6  $V_{CT}$  Analog Graph

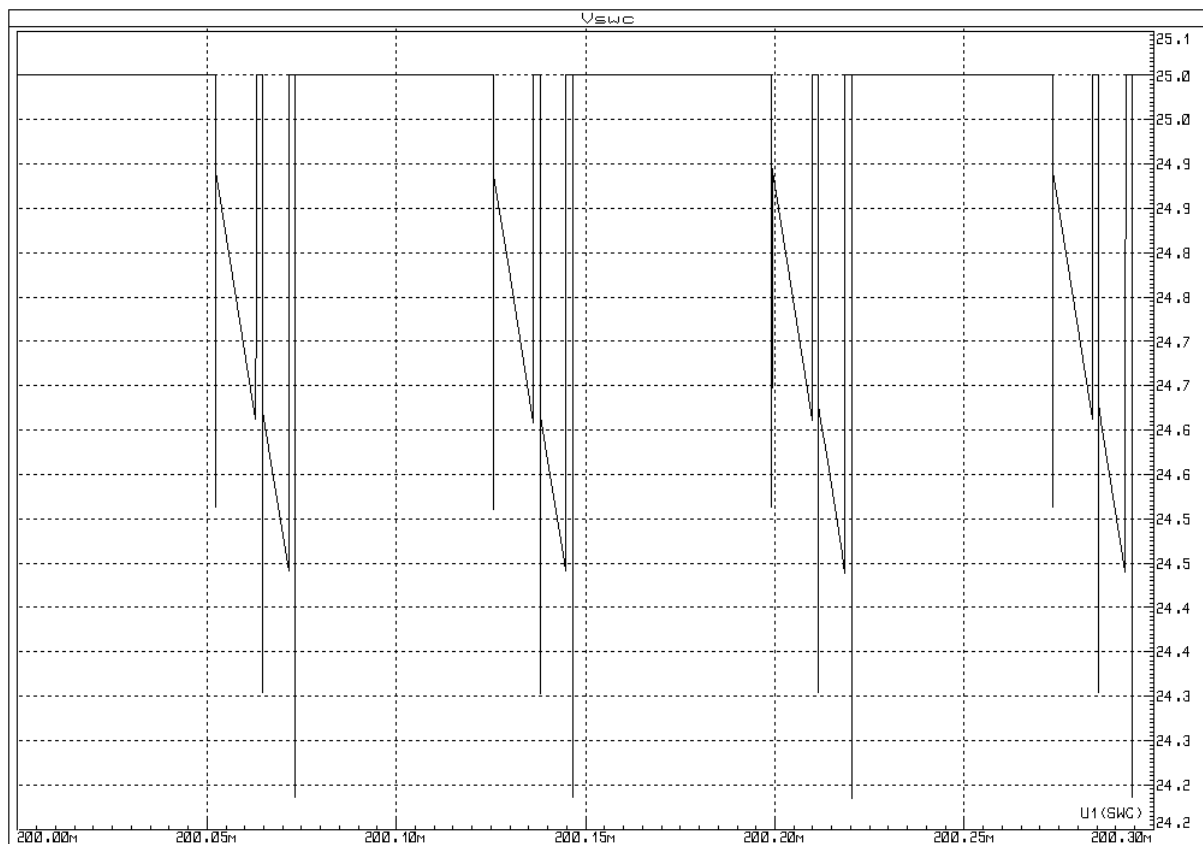


Figure 7  $V_{swc}$  Analog Graph

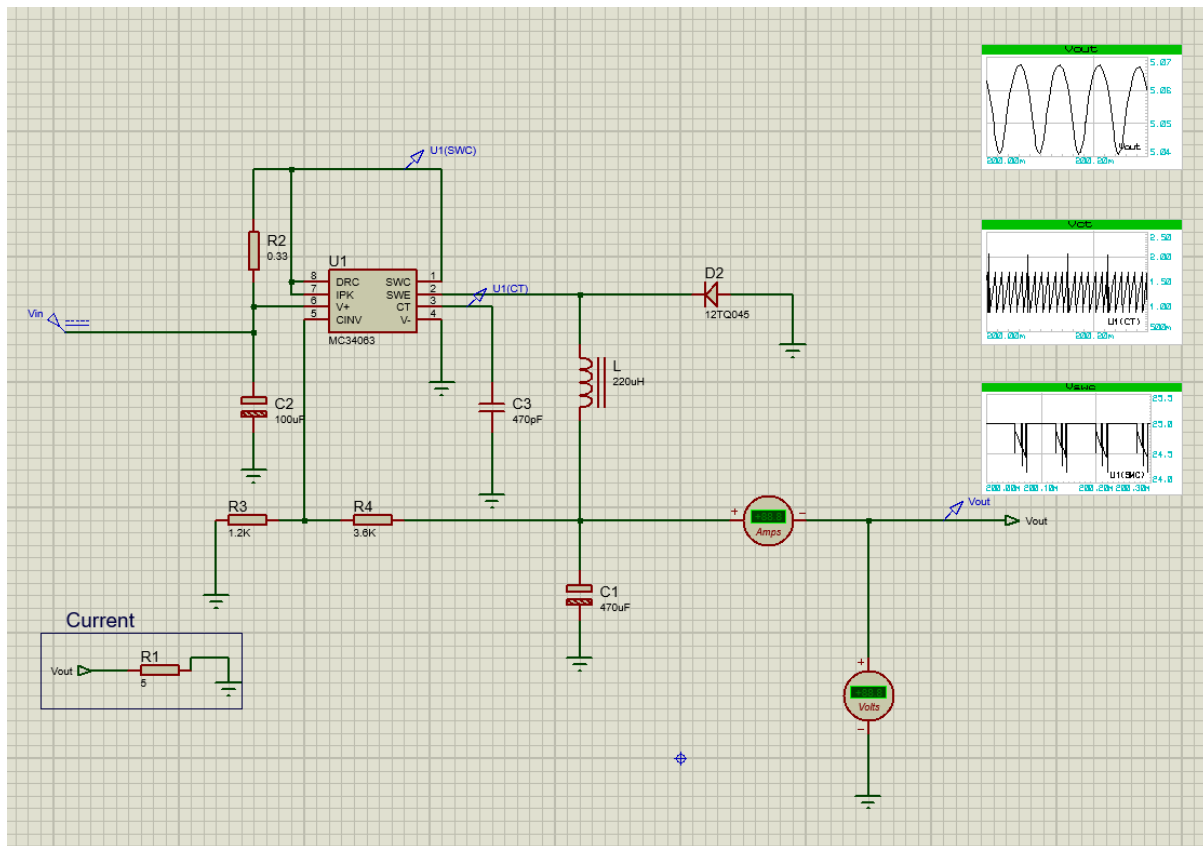


Figure 8 Step – down Analysis

## Step-up converter

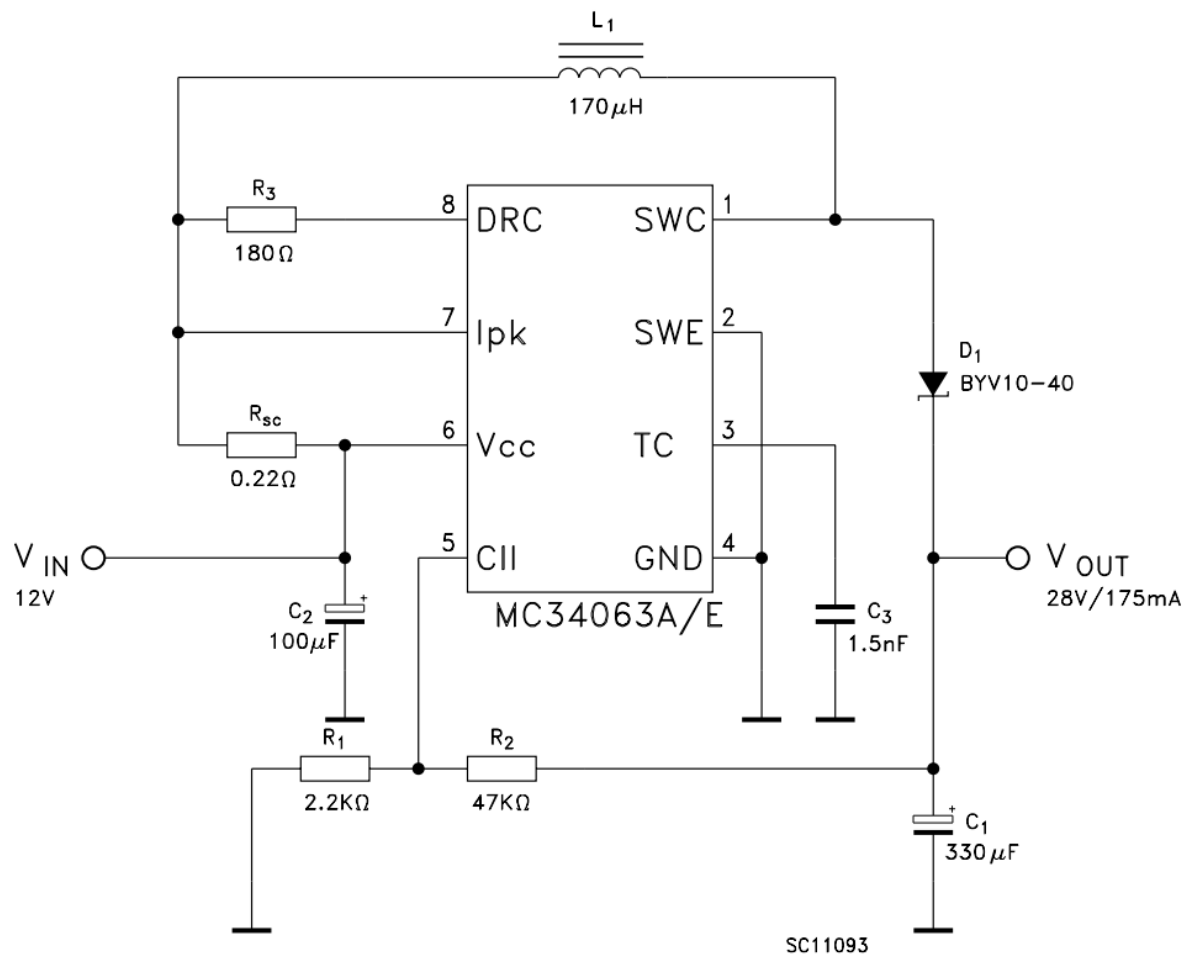


Figure 9 Step-up Converter Circuit of Datasheet

## Result

This is a MC 34063 step-up coverter circuit Proteus Diagram, input voltage ( $V_{in}$ ) is 12V, through the step-down circuit, the output voltage ( $V_{out}$ ) is 28V.

## Discussion

### Step-up converter circuit

Inverting Input of Comparator (Pin 5 CII) monitors the output voltage ( $V_{out}$ ) through two external voltage divide resistors  $R_1$  and  $R_2$ .  $V_{out} = 1.25 * (1 + \frac{R_2}{R_1})$ . From Figure 1, we know the reference voltage is 1.25V, it is constant. Pin 3 Timing capacitor recharged and discharged in order to produce oscillation. Recharging and discharging current is constant, oscillation frequency and switch on-off time depend on Pin 3 external timing capacitor. When Pin 5 input voltage larger than 1.25, Pin1 and Pin 2 turn on. Source recharged inductor and capacitor discharged the  $R_1$  and  $R_2$ . In contrast, Pin 2 and Pin1 turn off, inductor recharged capacitor  $R_1$  and  $R_2$ , since the electromotive force polarity at both ends is the same as the power supply polarity, equivalent to two power supplies connected in series, so output voltage over  $V_{in}$

Between Pin 6 and Pin7 external resistor ( $R_{SC}$ ), through testing resistor voltage drop realizes current limit. When testing resistor ( $R_{SC}$ ) voltage drop nears 0.3V, current limit circuit operates, through Pin 3 oscillation recharging timing capacitor quickly to reduce recharging time and Pin 2 switch turn on time, then extending Pin 2 switch turn off time. Pin 2 connect the GND.

### Step-up Diagram

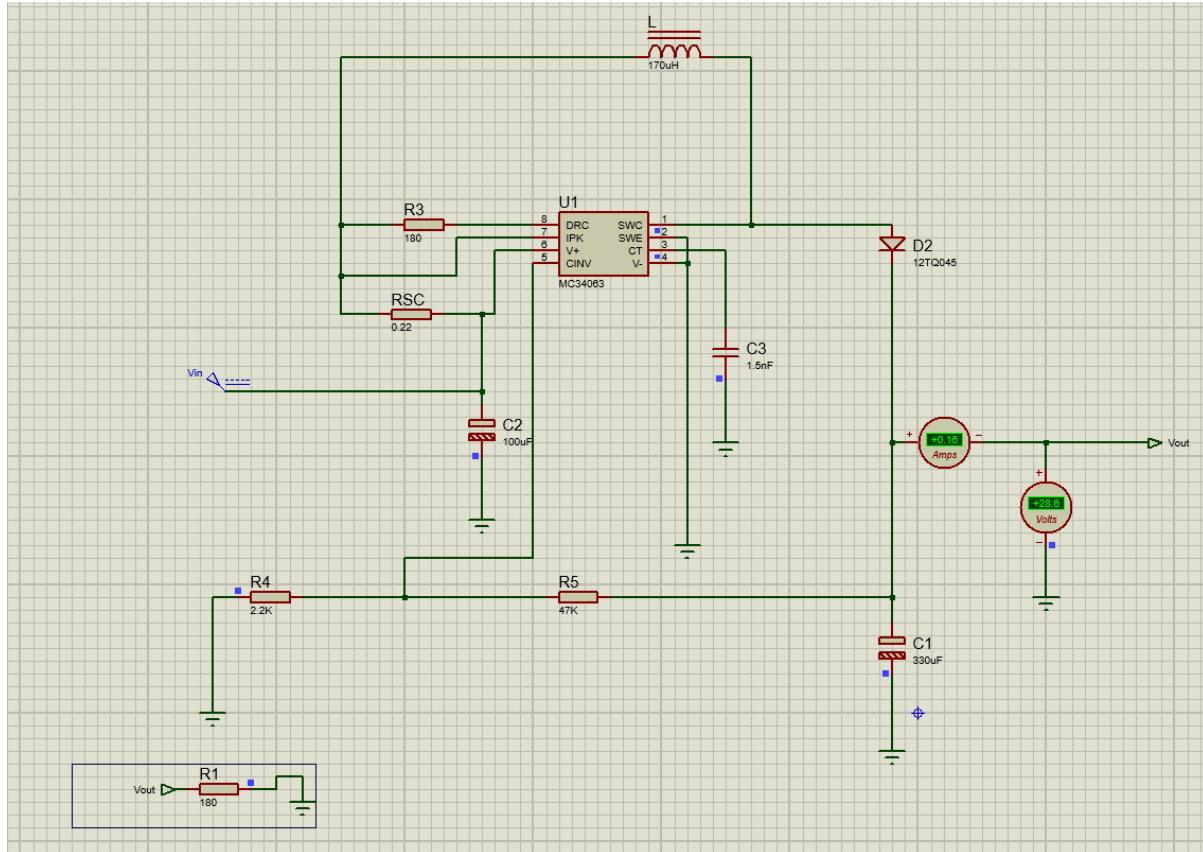


Figure 10 Step-up Diagram

### Results

This is a MC 34063 step-up converter circuit Proteus Diagram, input voltage ( $V_{in}$ ) is 12V, through the step-down circuit, the output voltage ( $V_{out}$ ) is 28.6V.

### Discussion

Inverting Input of Comparator (Pin 5 CII) monitors the output voltage ( $V_{out}$ ) through two external voltage divide resistors  $R_4$  and  $R_5$ .  $V_{out} = 1.25 * (1 + \frac{R_5}{R_4})$ . From Figure 1, we know the reference voltage is 1.25V, it is constant. Pin 3 Timing capacitor recharged and discharged in order to produce oscillation. Recharging and discharging current is constant, oscillation frequency and switch on-off time depend on Pin 3 external timing capacitor. When Pin 5 input voltage larger than 1.25, Pin1 and Pin 2 turn on. Source recharged inductor and capacitor discharged the  $R_4$  and  $R_5$ . In contrast, Pin 2 and Pin1 turn off, inductor recharged capacitor  $R_4$  and  $R_5$ , since the electromotive force polarity at both ends is the same as the power supply polarity, equivalent to two power supplies connected in series, so output voltage over  $V_{in}$

Between Pin 6 and Pin7 external resistor ( $R_{SC}$ ), through testing resistor ( $R_{SC}$ ) voltage drop realizes current limit. When testing resistor voltage drop nears 0.3V, current limit circuit operates, through Pin 3 oscillation recharging timing capacitor quickly to reduce recharging time and Pin 2 switch turn on time, then extending Pin 2 switch turn off time. Pin 2 connect the GND.

From Figure 11, 12, 13. When time = 0, switch turn off, inductor recharged capacitor  $R_4$  and  $R_5$ , since the electromotive force polarity at both ends is the same as the power supply polarity, equivalent to two power supplies connected in series, so output voltage over  $V_{in}$ ,  $V_{out}$  increased. When time = 4.691ms,  $V_{out} = 28.6V$ ,  $V_{CT} = 1.29V$ ,  $V_{SWC} = 29V$ , switch turn on, source recharged inductor and capacitor discharged the  $R_4$  and  $R_5$ ,  $V_{out}$  begins drop, switch turn off again.


$$T_{on} = \frac{C_T}{4.5 \times 10^{-5}}$$

$$T_{on} = \frac{1.5 \times 10^{-9}}{4.5 \times 10^{-5}}$$

$$T_{on} = \frac{1.5 \times 10^{-9}}{4.5 \times 10^{-5}} = 33 \mu s$$

$$V_{ripple} = \frac{I_{out} \cdot T_{on}}{C_o}$$

$$V_{ripple} = \frac{0.175 \cdot 33 \times 10^{-6}}{330 \times 10^{-6}} = 0.0175V$$

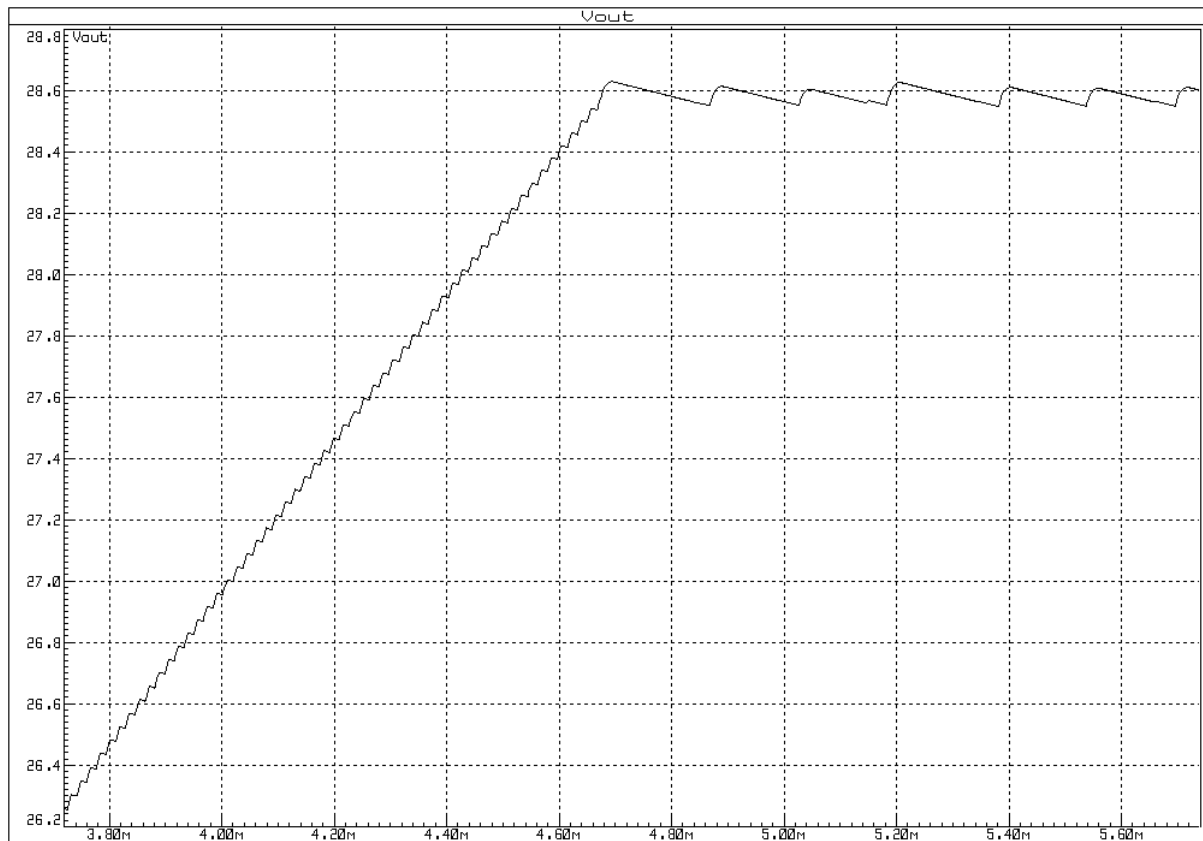

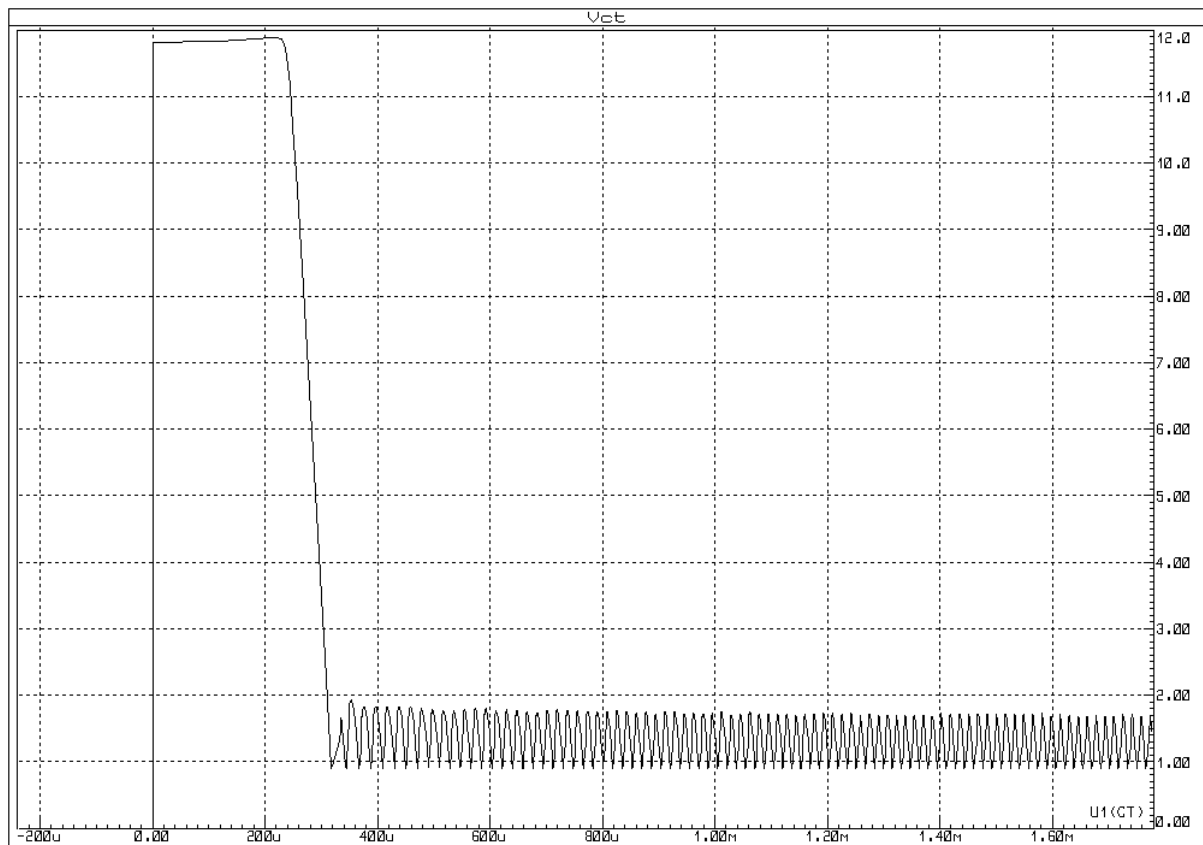
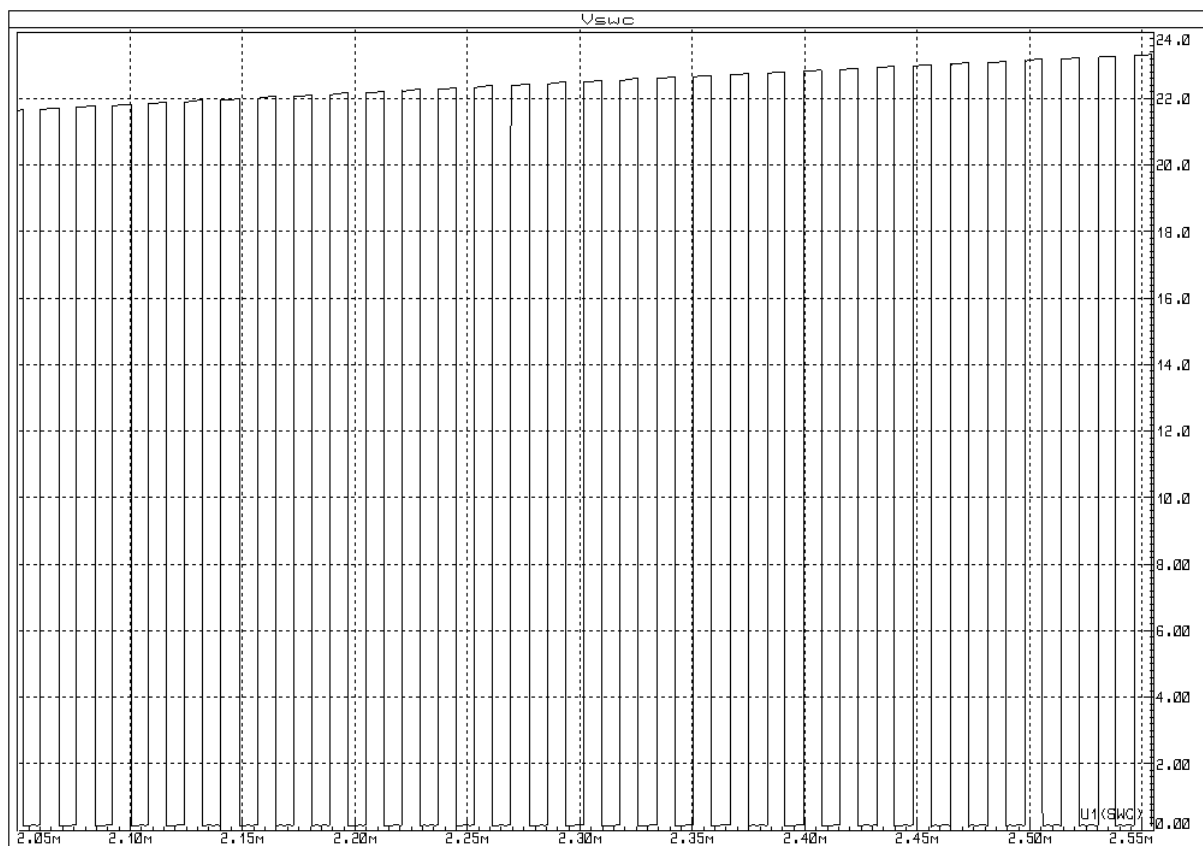
*Figure 11  $V_{out}$  Analog Graph**Figure 12  $V_{CT}$  Analog Graph*

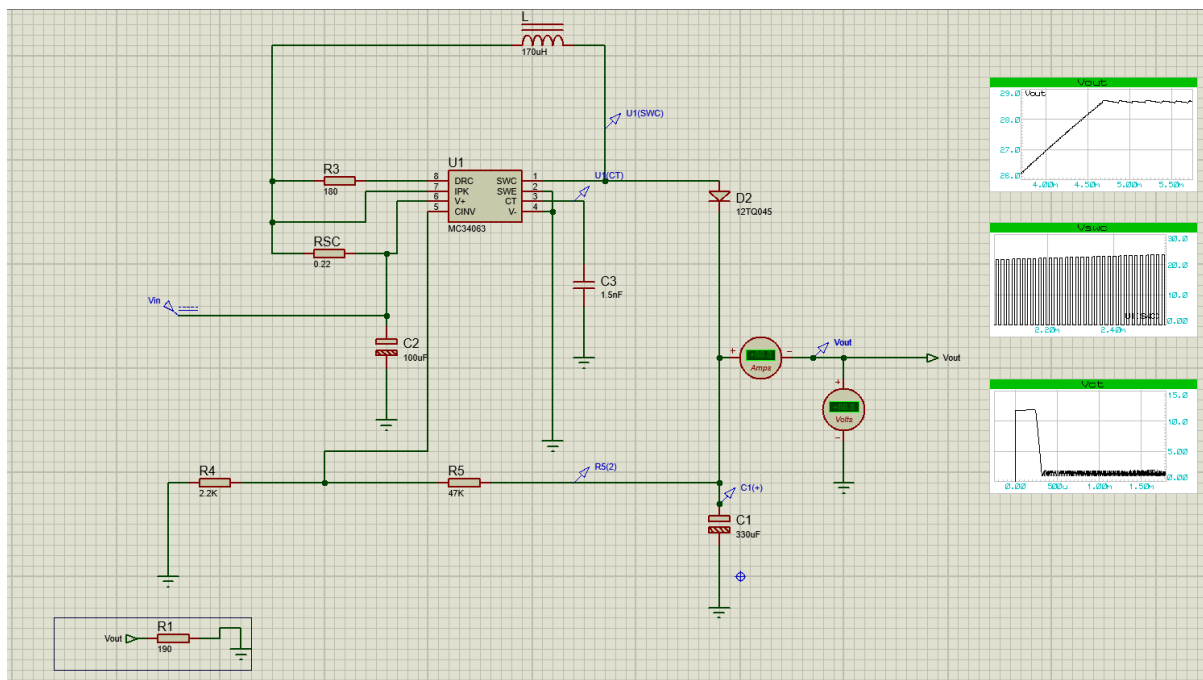
Figure 13  $V_{ripple}$  Analog Graph

Figure 14 Step – up Analysis

## Buck Converter Design

Design a buck converter select output current value in range of 200mA to 500mA, output voltage under 12V.  $V_{in} = 10V$   $V_{out} = 5V$ .  $f = 40kHz$ .  $V_{ripple} = 100mV(pp)$

If we check the datasheet, we can see the complete formula chart is present to calculate the desired values required as per our requirement. Here is the formula sheet available inside the datasheet, and the step-down circuit is also shown.

**Calculation**

Parameter	Step-Up (Discontinuous mode)	Step-Down (Continuous mode)	Voltage Inverting (Discontinuous mode)
$t_{on}/t_{off}$	$\frac{V_{out} + V_F - V_{in(min)}}{V_{in(min)} - V_{sat}}$	$\frac{V_{out} + V_F}{V_{in(min)} - V_{sat} - V_{out}}$	$\frac{ V_{out}  + V_F}{V_{in} - V_{sat}}$
$(t_{on} + t_{off})_{max}$	$1/f_{min}$	$1/f_{min}$	$1/f_{min}$
$C_T$	$4.5 \times 10^{-5} t_{on}$	$4.5 \times 10^{-5} t_{on}$	$4.5 \times 10^{-5} t_{on}$
$I_{PK(switch)}$	$2I_{out(max)}[(t_{on}/t_{off}) + 1]$	$2I_{out(max)}$	$2I_{out(max)}[(t_{on}/t_{off}) + 1]$
$R_{sc}$	$0.3/I_{PK(switch)}$	$0.3/I_{PK(switch)}$	$0.3/I_{PK(switch)}$
$C_o$	$\equiv \frac{I_{out} t_{on}}{V_{ripple(p-p)}}$	$\frac{I_{PK(switch)} (t_{on} + t_{off})}{8V_{ripple(p-p)}}$	$\equiv \frac{I_{out} t_{on}}{V_{ripple(p-p)}}$
$L_{(min)}$	$\frac{V_{in(min)} - V_{sat}}{I_{PK(switch)}} t_{on(max)}$	$\frac{V_{in(min)} - V_{sat} - V_{out}}{I_{PK(switch)}} t_{on(max)}$	$\frac{V_{in(min)} - V_{sat}}{I_{PK(switch)}} t_{on(max)}$

**NOTES:**

$V_{sat}$  = Saturation voltage of the output switch

$V_F$  = Forward voltage drop of the output rectifier

THE FOLLOWING POWER SUPPLY CHARACTERISTICS MUST BE CHOSEN:

$V_{in}$  = Nominal input voltage

$V_{out}$  = Desired output voltage,  $|V_{out}| = 1.25(1 + R_2/R_1)$

$I_{out}$  = Desired output current

$f_{min}$  = Minimum desired output switching frequency at the selected values of  $V_{in}$  and  $I_o$

$V_{ripple}$  = Desired peak to peak output ripple voltage. In practice, the calculated capacitor value will need to be increased due to its equivalent series resistance and board layout. The ripple voltage should be kept to a low value since it will directly affect the line and load regulation.

*Figure 15 Formula Calculation*

**OUTPUT SWITCH**

Symbol	Parameter	Test Conditions	Min.	Typ.	Max.	Unit
$V_{CE(sat)}$	Saturation Voltage, Darlington Connection	$I_{SW} = 1 \text{ A}$ Pins 1, 8 connected		1	1.3	V
$V_{CE(sat)}$	Saturation Voltage	$I_{SW} = 1 \text{ A}$ $R_{pin8} = 82 \Omega$ to $V_{CC}$ , Forced $\beta \sim 20$		0.45	0.7	V
$h_{FE}$	DC Current Gain	$I_{SW} = 1 \text{ A}$ $V_{CE} = 5 \text{ V}$ $T_a = 25^\circ \text{C}$	50	120		
$I_{C(off)}$	Collector Off-State Current	$V_{CE} = 40 \text{ V}$		0.01	100	$\mu\text{A}$

*Figure 16 MC34063 datasheet- Saturation Voltage*

$V_{sat} \text{ Typ.} = 1$ , so we make  $V_{sat} = 1 \text{ V}$

We will use 12TQ045 diode, from this datasheet, so we make  $V_F = 0.35 \text{ V}$

Step 1: First, we need to select the Diode. We will choose widely available diode 12TQ045. As per the datasheet, at 1A forward current the forward voltage of the diode will be 0.35 V.



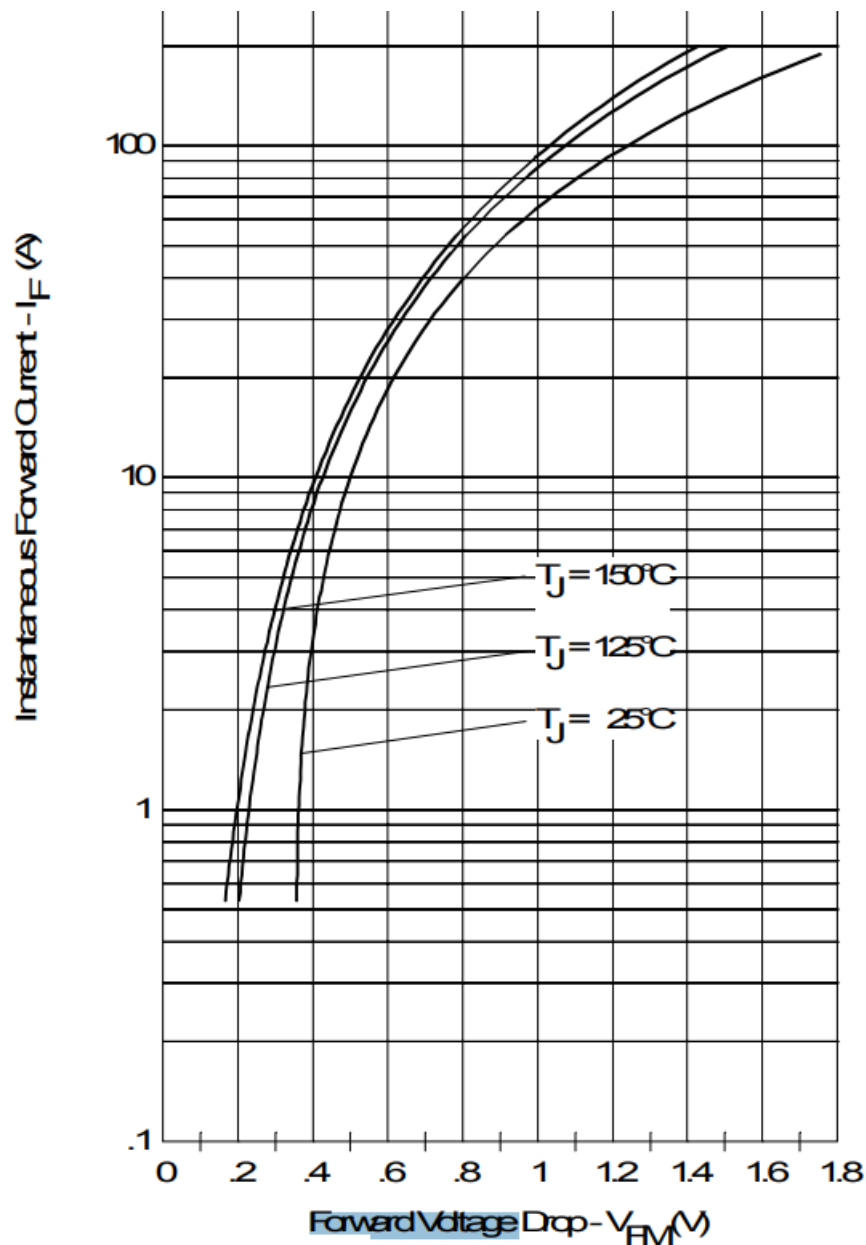


Fig. 1 - Maximum Forward Voltage Drop Characteristics

Figure 17 12TQ045 diode datasheet - Forward voltage

Step 2: We will calculate the  $T_{on}/T_{off}$  using the formula below:

$$\frac{T_{on}}{T_{off}} = \frac{V_{out} + V_F}{V_{in(min)} - V_{sat} - V_{out}}$$

$$\frac{T_{on}}{T_{off}} = \frac{5V + 0.5V}{10V - 1V - 5V}$$

$$\frac{T_{on}}{T_{off}} = 1.34$$

$$T_{on} = 1.34 * T_{off}$$

Step 3: Now we will calculate the  $T_{on} + T_{off}$  time, as per the formula  $T_{on} + T_{off} = 1 / f$

We will select a lower switching frequency, 40kHz.

$$T_{on} + T_{off} = \frac{1}{f}$$

$$T_{on} + T_{off} = \frac{1}{40 * 10^3} = 25 \text{ us}$$

Step 4: Now we will calculate the  $T_{off}$  time. As we calculated the  $T_{on} + T_{off}$  and  $\frac{T_{on}}{T_{off}}$  previously, the calculation will be easier now

$$1.34 * T_{off} + T_{off} = 25 \text{ us}$$

$$T_{off} = 10.68$$

Step 5: Now the next step is to calculate  $T_{on}$

$$T_{on} = 14.32$$

Step 6: We need to choose the timing Capacitor  $C_T$ , which will be required to produce the desired frequency

$$C_T = 4.5 * 10^{-5} * T_{on}$$

$$C_T = 4.5 * 10^{-5} * 14.32$$

$$C_T = 644 \text{ pF we can use } 680 \text{ pF}$$

Step 7: The Switching peak current

$$I_{pk(\text{switch})} = 2 * I_{out(\text{max})}$$

$$I_{pk(\text{switch})} = 2 * 500 \text{ mA}$$

$$I_{pk(\text{switch})} = 1 \text{ A}$$

Step 8: For the  $R_{sc}$  value will be  $0.3 / I_{pk(\text{switch})}$

$$R_{sc} = \frac{0.3}{I_{pk(\text{switch})}}$$

$$R_{sc} = 0.3$$

Step 9: Depending on those values we will calculate the Inductor value

$$L_{min} = \frac{V_{in(\text{min})} - V_{sat} - V_{out}}{I_{pk(\text{switch})}} * T_{on}$$

$$L_{min} = \frac{10 \text{ V} - 1 \text{ V} - 5 \text{ V}}{1} * 14.32$$

$$L_{min} = 57.28 \text{ uH we can use } 100 \text{ uH}$$

Step 10: Let's calculate the output capacitor values, we can choose a ripple value of 100mV (peak to peak) from the boost output.

$$C_o = \frac{I_{pk(\text{switch})} * (T_{on} + T_{off})}{8 * V_{ripple}}$$

$$C_o = \frac{1 * 25}{8 * 10 * 10^{-3}} = 31 \text{ uF we can use } 33 \text{ uF}$$

Step 11: Last we need to calculate the voltage feedback resistors value. We will choose R1 value 1k, So, the R2 value will be calculated as

$$V_{out} = 1.25 * (1 + \frac{R_2}{R_1})$$

$$R_1 = 1K, R_2 = 3K$$

Component	Value	Unit	Select	Unit
$C_T$	644	pF	680	pF
$R_{Sc}$	0.3	ohms	0.33	ohms
$L_{min}$	57.28	uH	100	uH
$C_o$	31	uF	33	uF
$R_3$	1K	ohms	1K	ohms
$R_4$	3K	ohms	3K	Ohms
$C_1$	/	/	100	uF

Chart2 Component value

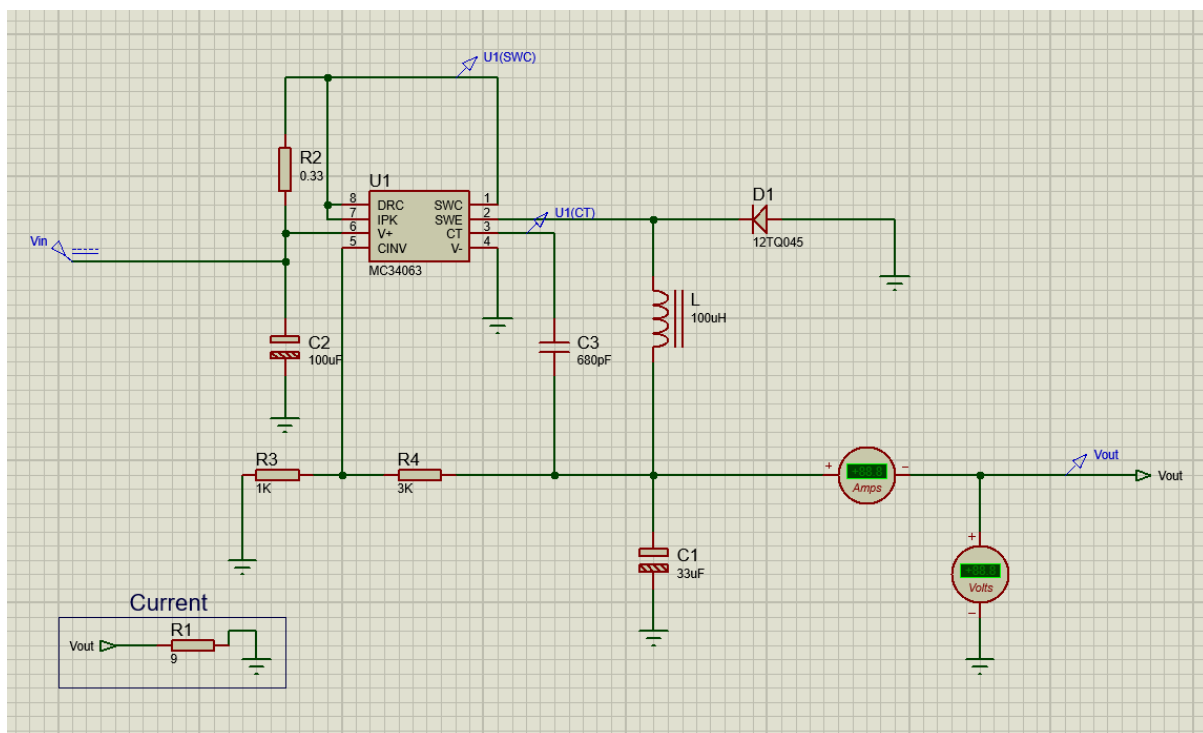


Figure18 Buck Converter

## Results

This is a MC 34063 new design buck coverter circuit Proteus Diagram, input voltage ( $V_{in}$ ) is 10V, through the step-down circuit, the output voltage ( $V_{out}$ ) is 5.07V.

☑ Capacitor  $C_2$ , since input voltage is 10V, the withstand voltage must be greater than 12V, double the input voltage here.

☑  $R_{sc} = R_2$  is current limit resistor. It adjusted output load current and when between Pin 6 and Pin 7 voltage over 165mV, internal current limit function will be opened.

☑ Capacitor  $C_T$  connect with GND, it determines operating frequency.

☑ Diode  $D_1$ , we use fast switch diode, but for high efficiency application, the Schottky diode must be used.

☑ Inductance  $L$ , energy storage.

☑  $R_1=R_3, R_2=R_4$ , feedback circuit. They determine output voltage.

☑ Capacitor  $C_1 = C_o$ , output capacitor, the within voltage is OK.

☑  $R_5$  is discharge resistor, the value is larger, discharge is slower.

### Discussion

Inverting Input of Comparator (Pin 5 CII) monitors the output voltage ( $V_{out}$ ) through two external voltage divide resistance (  $R_3$  and  $R_4$  )  $V_{out} = 1.25*(1+\frac{R_4}{R_3})$ , from Figure 1, we know the reference voltage is 1.25V, it is constant. Pin 3 Timing capacitor recharged and discharged in order to produce oscillation. Recharging and discharging current is constant, oscillation frequency depends on Pin 3 external timing capacitor. When Pin 5 input voltage larger than 1.25, Pin1 and Pin 2 turn on. Source recharge  $C_1$  and  $L$ ,. In contrast, Pin 2 and Pin1 turn off, the inductor ( $L$ ) recharged capacitor ( $C_1$ ).

Between Pin 6 and Pin7 is  $R_2$ , through testing  $R_2$  voltage drop realizes current limit. When testing  $R_2$  voltage drop nears 0.1V, current limit circuit operates, through Pin 3 oscillation recharging timing capacitor quickly, reducing recharging time and Pin 2 switch turn on time, then extending Pin 2 switch turn off time, Pin 8 and Pin 2 external resistor and inductor to prevent higher voltage.

From the Figure 19 and Figure 21, when time =200.072ms,  $V_{CT} = 1.05V$ ,  $V_{out} = 4.88V$ ,  $V_{swc} = 9.82V$ , switch turn on, source ( $V_{in}$ ) recharge  $C_1$  and  $L$ ,  $V_{out}$  increased. When time =200.084ms,  $V_{CT} = 1.69V$ ,  $V_{out} = 4.94V$ ,  $V_{swc} = 9.71V$ , since  $R_2$  voltage drop = 9.81-9.71=0.1V nears 0.1V, current limit circuit operates, through Pin 3 oscillation recharging timing capacitor quickly to reduce recharging time and Pin 2 switch turn on time, then extending Pin 2 switch turn off time,  $V_{out}$  continues increased. When time = 200.107ms,  $V_{CT} = 1.19V$ ,  $V_{swc} = 10V$ ,  $V_{out} = 5.16V$ , switch turn off,  $V_{out}$  suddenly drop (between time=200.107ms and time= 200.111ms), since switch suddenly turn off,  $V_{out}$  suddenly drop,  $L$  begins to recharge  $C_1$ ,  $V_{out}$  slowly drop. When time=200.146ms,  $V_{CT} = 1.09V$ ,  $V_{out} = 4.88V$ ,  $V_{swc} = 9.82V$ , switch turn on, source ( $V_{in}$ ) recharge  $C_1$  and  $L$ ,  $V_{out}$  increased.

$$T_{on} + T_{off} = 1 / (200.069-200.029) = 25 \text{ (from Figure 20)}$$

$$V_{ripple} = \frac{I_{pk( switch )} * (T_{on} + T_{off})}{8 * C_o}$$

$$V_{ripple} = \frac{1 * 25}{8 * 33} = 95 \text{ mV}$$

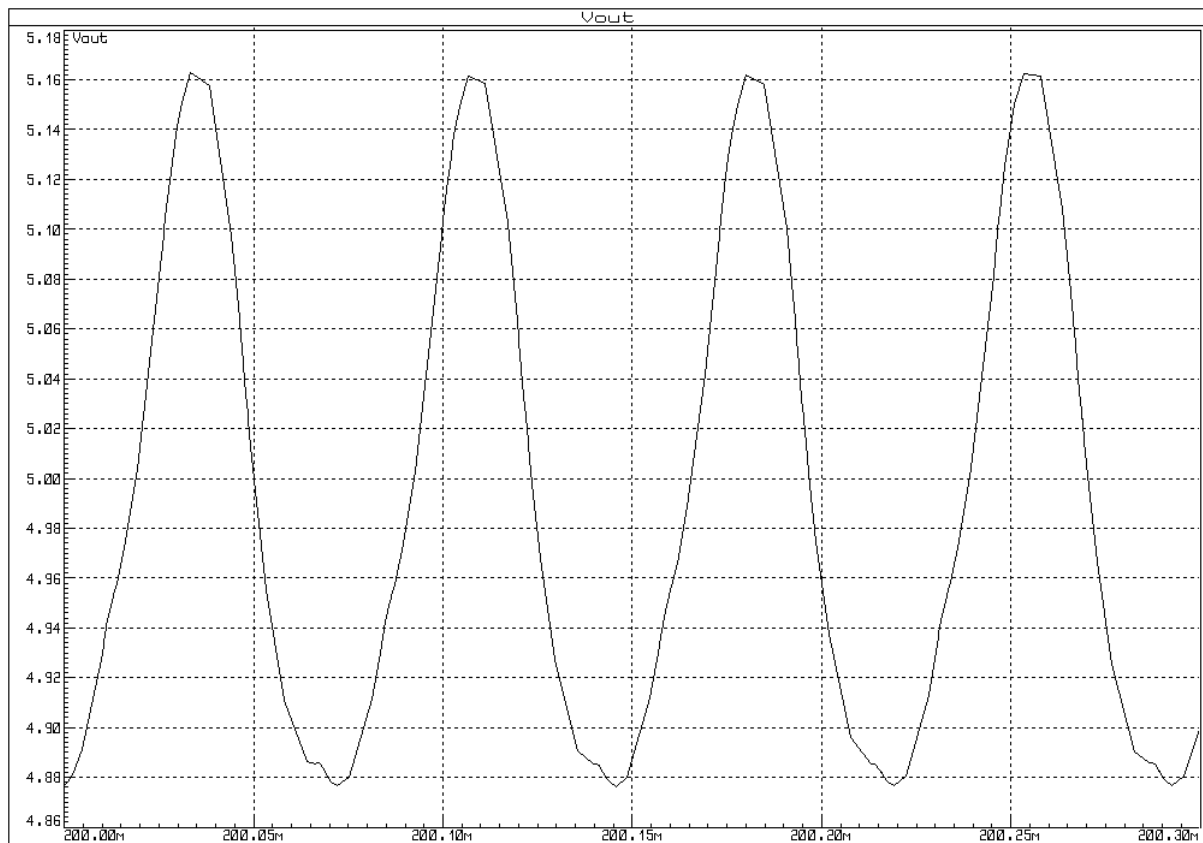


Figure 19  $V_{out}$  Analog Graph

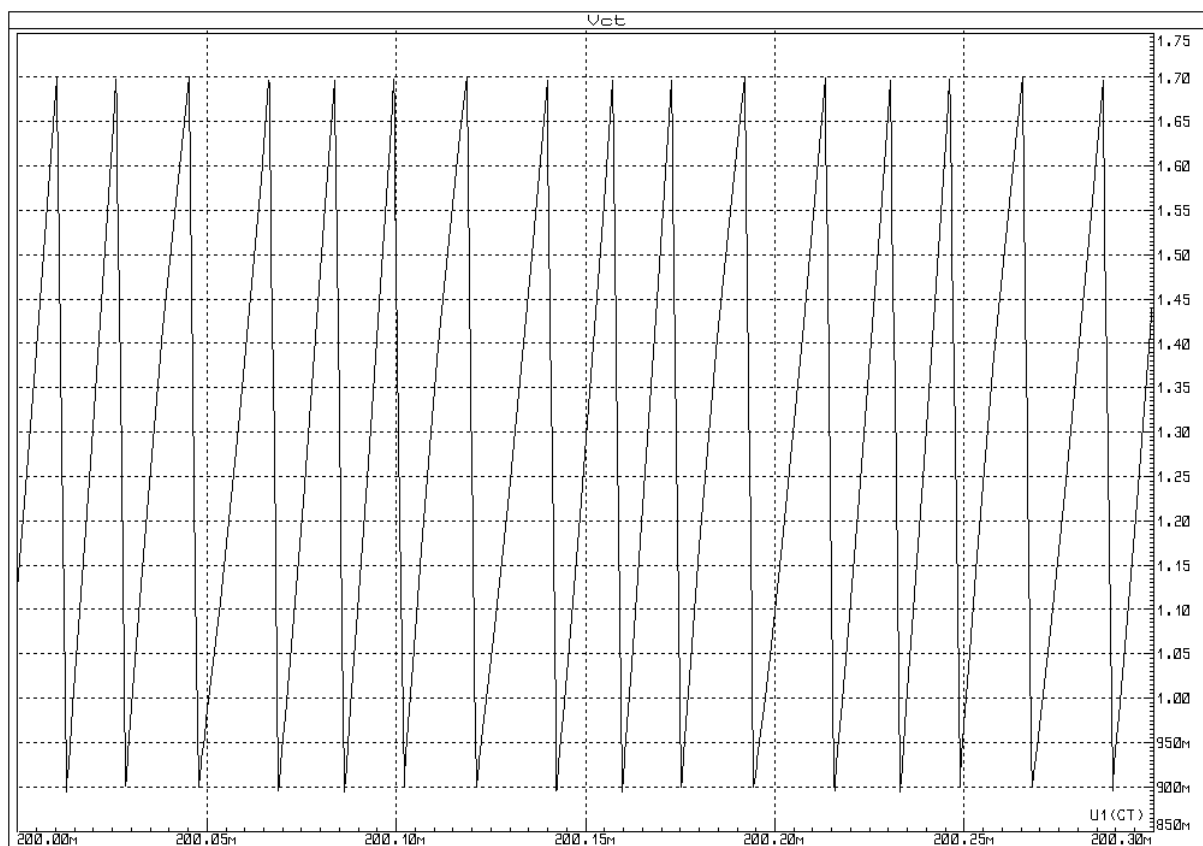


Figure 20  $V_{ct}$  Analog Graph

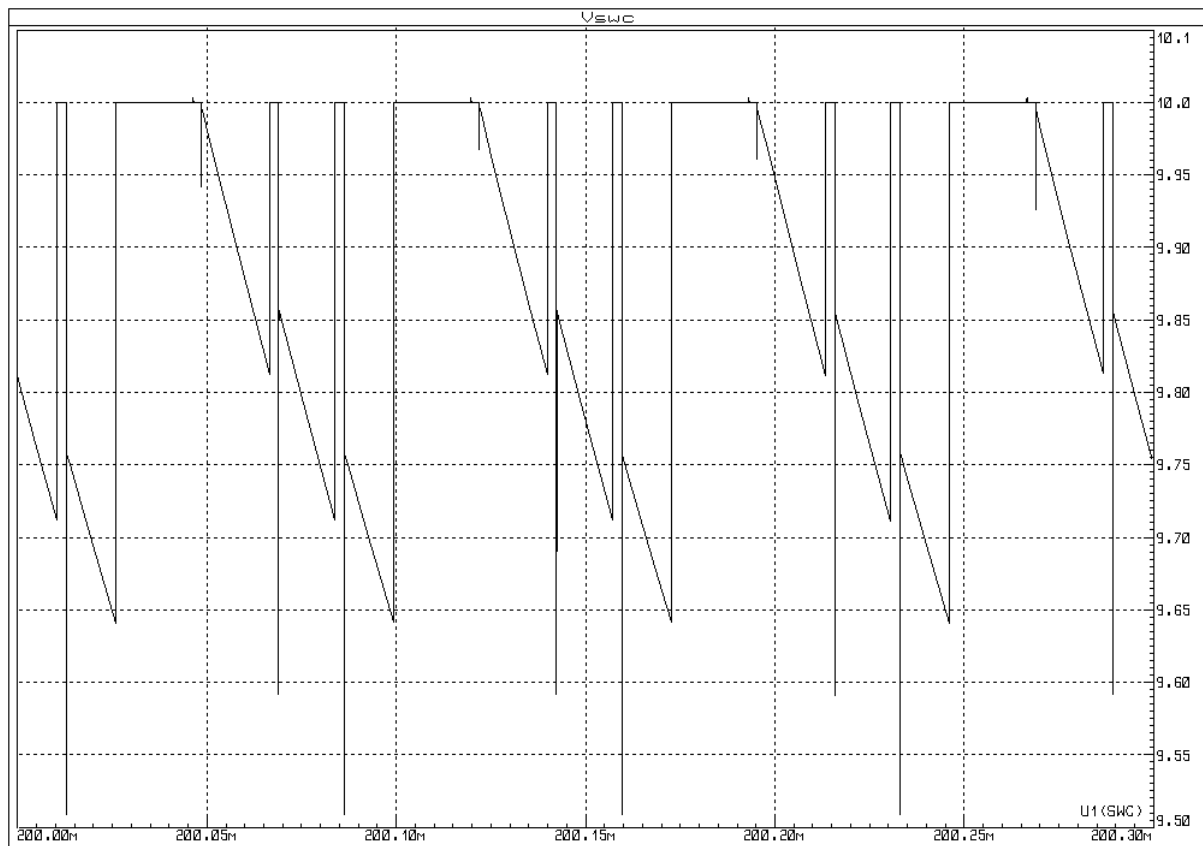


Figure 21  $V_{swc}$  Analog Graph


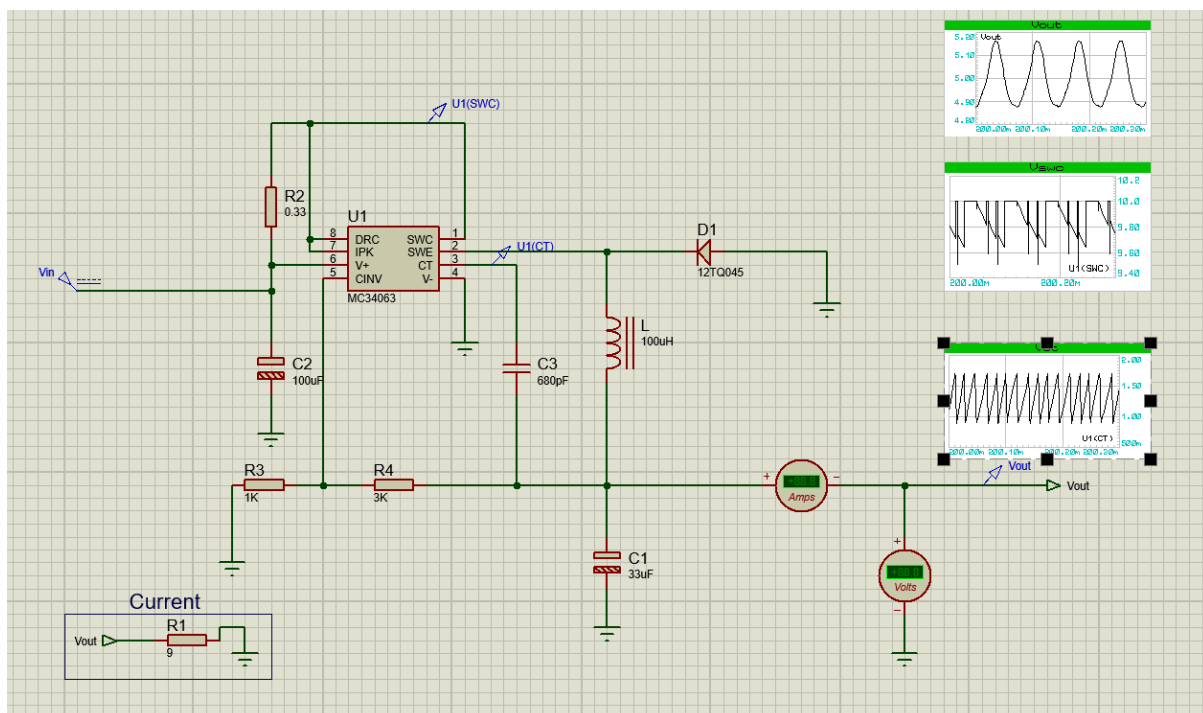



Figure 22 Buck converter Analysis

## Buck Converter Circuit

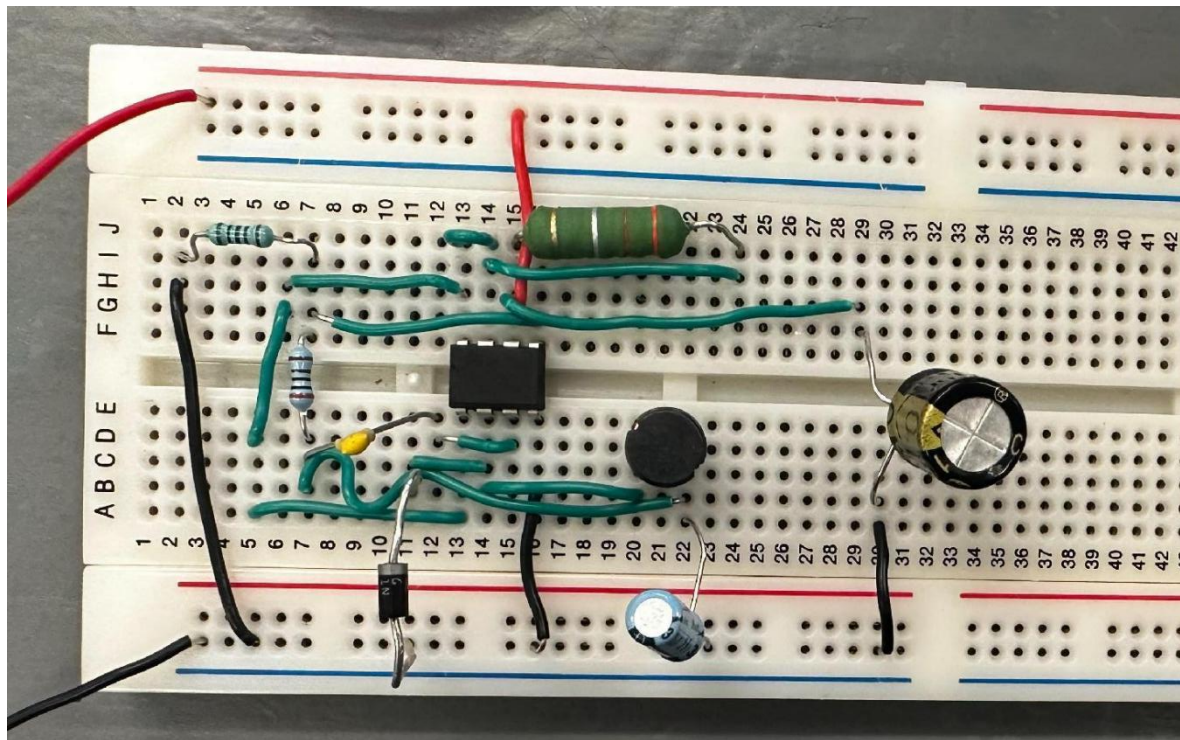


*Figure 23 Buck Converter Circuit*


From Figure 24, this is pin3 Voltage, we can see the frequency is 36.44kHz, PK-PK voltage is 1.06V.

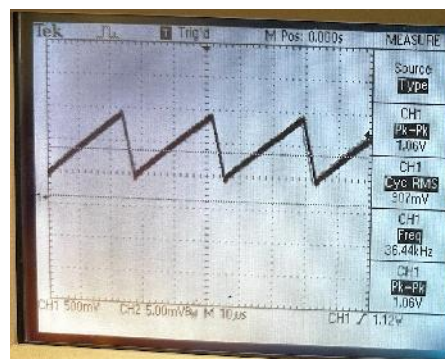

*Figure 24 Frequency*

From Figure 25, this is pin2 voltage, that is the output voltage we can see the voltage ( $V_{out}$ ) is 5.2V, ripple voltage ( $V_{ripple}$ ) is 0.2V.

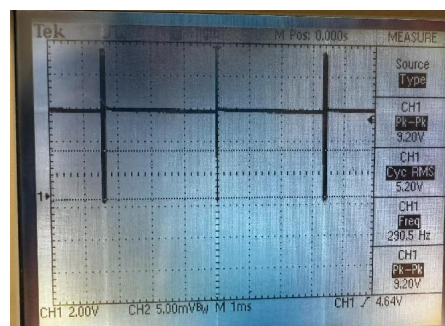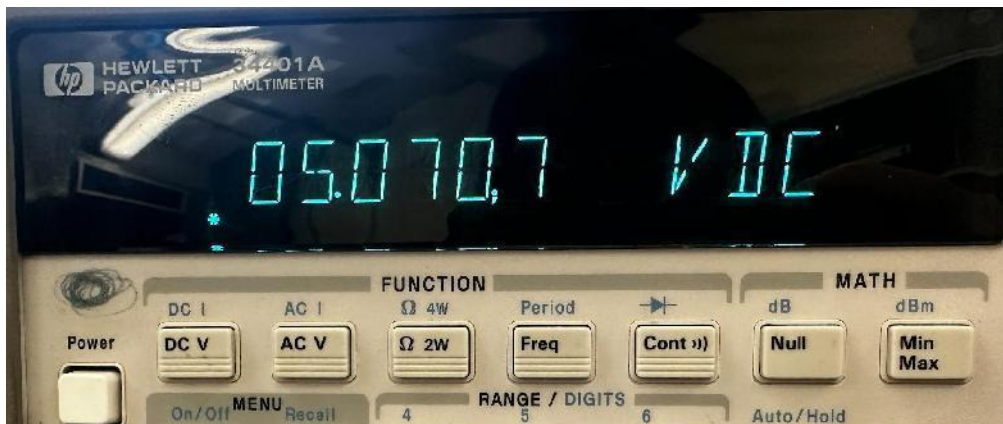

*Figure 25  $V_{ripple}$* *Figure 26  $V_{out}$  Tested Value = 5V*



## Conclusions

### Reflections

This report analyses the DC-DC Buck converter is its ability to act as a voltage regulator, using MC34063 IC to control the flow of current to the load. It is widely used in applications that require a steady, reliable output voltage.

We through test and simulate step up/down converter circuit and know MC34063 internal operating structure.

- ☑ This IC provides following features in its 8 pins package
- ☑ High efficiency adjustable output voltage, especially important for battery-operated equipment that needs to run for long periods of time.
- ☑ Adjustable switching frequency. Can be operated at 100 kHz switching frequency with a 2% tolerance.
- ☑ Temperature compensated reference
- ☑ Current limit circuit
- ☑ Controlled Duty cycle oscillator with an active high current driver output switch.
- ☑ Wide input voltage range: accept 3.0V to 40V DC.
- ☑ Very low Standby current
- ☑ Simply design circuit. It saved too much time.
- ☑ Wide range of applications: MC34063 can be used in a variety of applications, including power supplies, LED drivers, chargers, voltage regulators and other occasions requiring power management.
- ☑ Also, despite these features, it is widely available and it is much cost efficient than other ICs available in such segment.

### Referencing

*circuitdigest.com. (n.d.). 12V to 5V Buck Converter Circuit using MC34063. [online]*  
Available at: <https://circuitdigest.com/electronic-circuits/12v-to-5v-buck-converter-circuit-diagram>

*digchip.com. (n.d.). datasheet 12TQ045. [online]* Available at:  
<https://digchip.com/datasheets/parts/datasheet/232/12TQ045-pdf>